

# Low Noise Preamplifier and Our Blue Print

Anyi Rao

# Project requirements

- Voltage Gain  $A_v \geq 100$ 
  - Plan 1:  $A_v = 1500$
  - Plan 2:  $A_v = 2000$
- Band width  $BW = 1\text{k Hz}$
- Central frequency  $f = 4\text{k Hz}$
- low noise  $RTI \leq 5 \mu\text{V}$


Selection of  
component




Arrangement

Amplifier  
and filter


# Plan 1

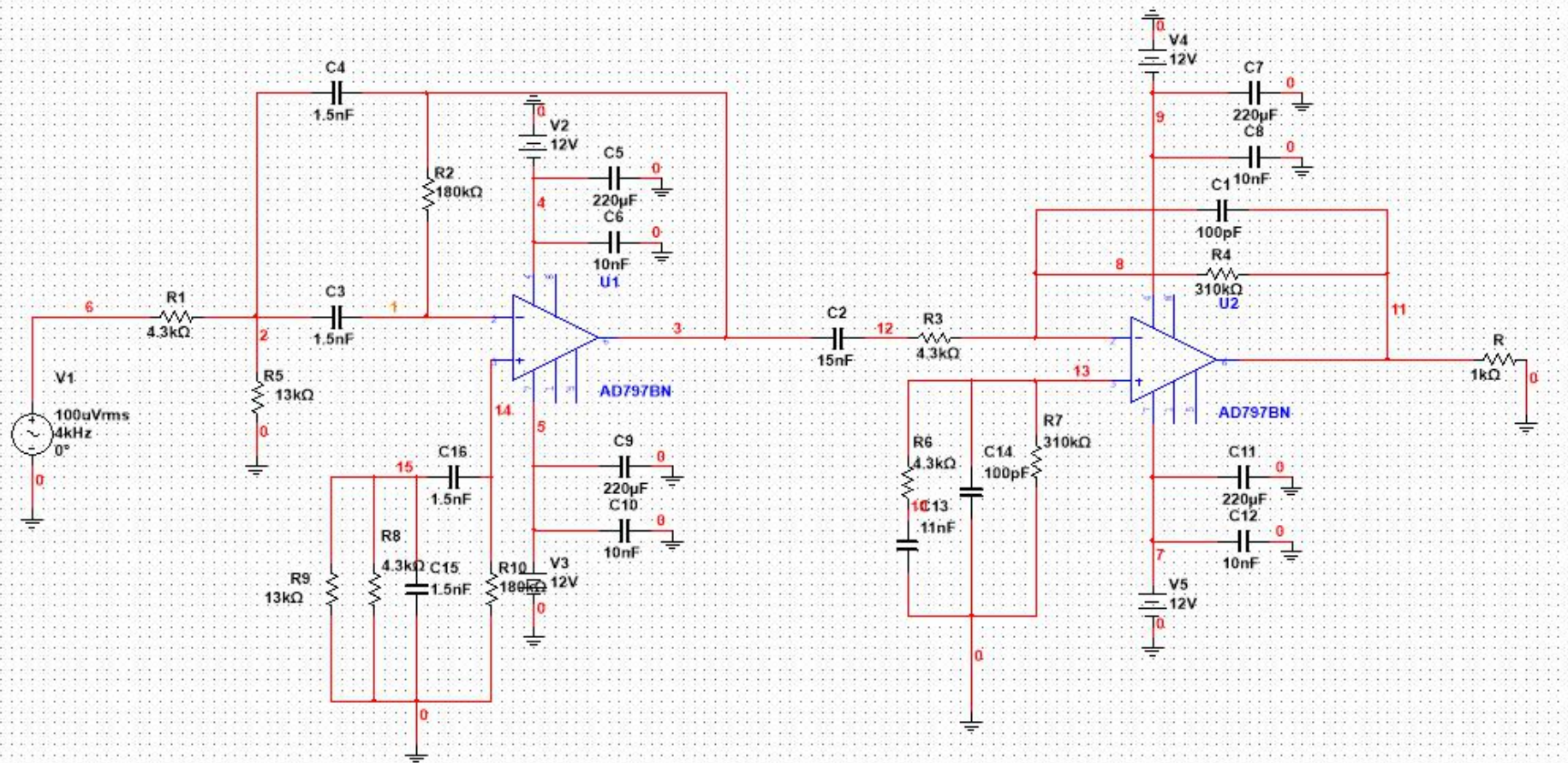

# Plan 1

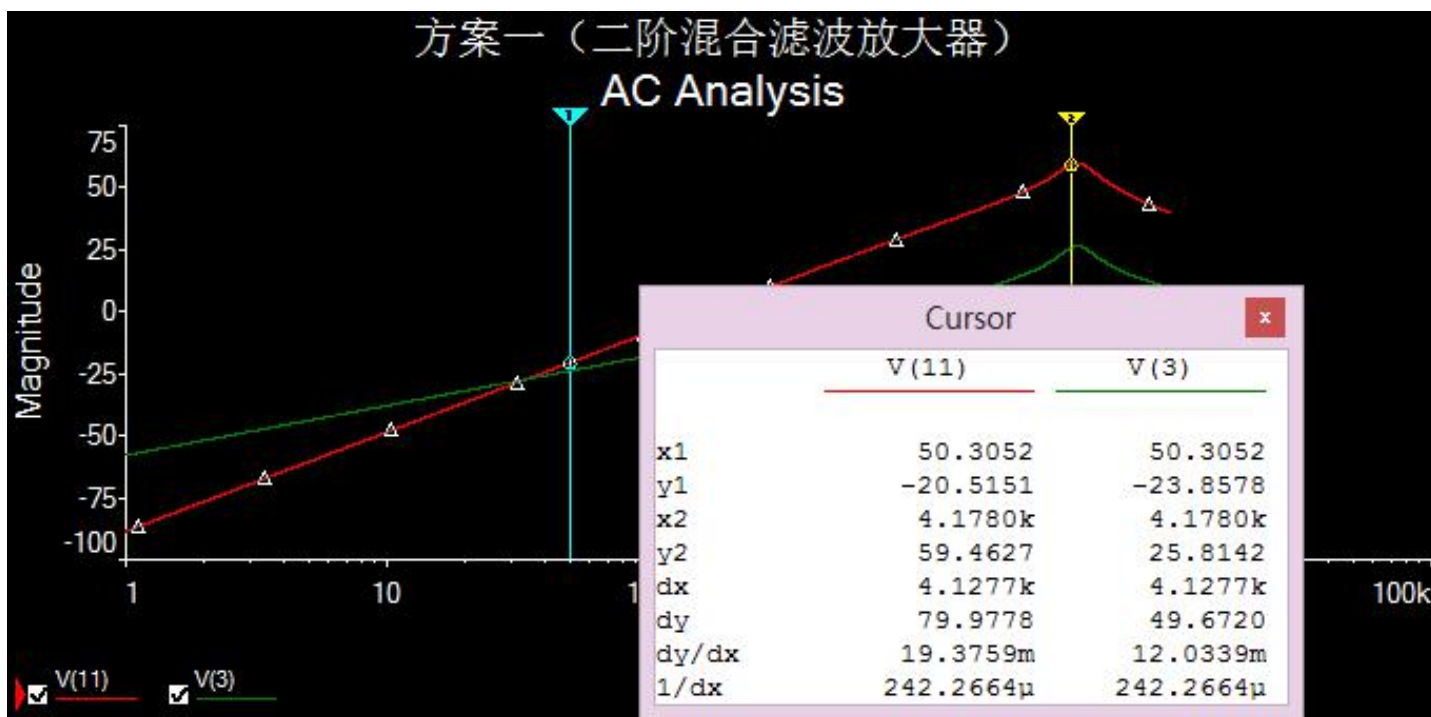


# Plan 2

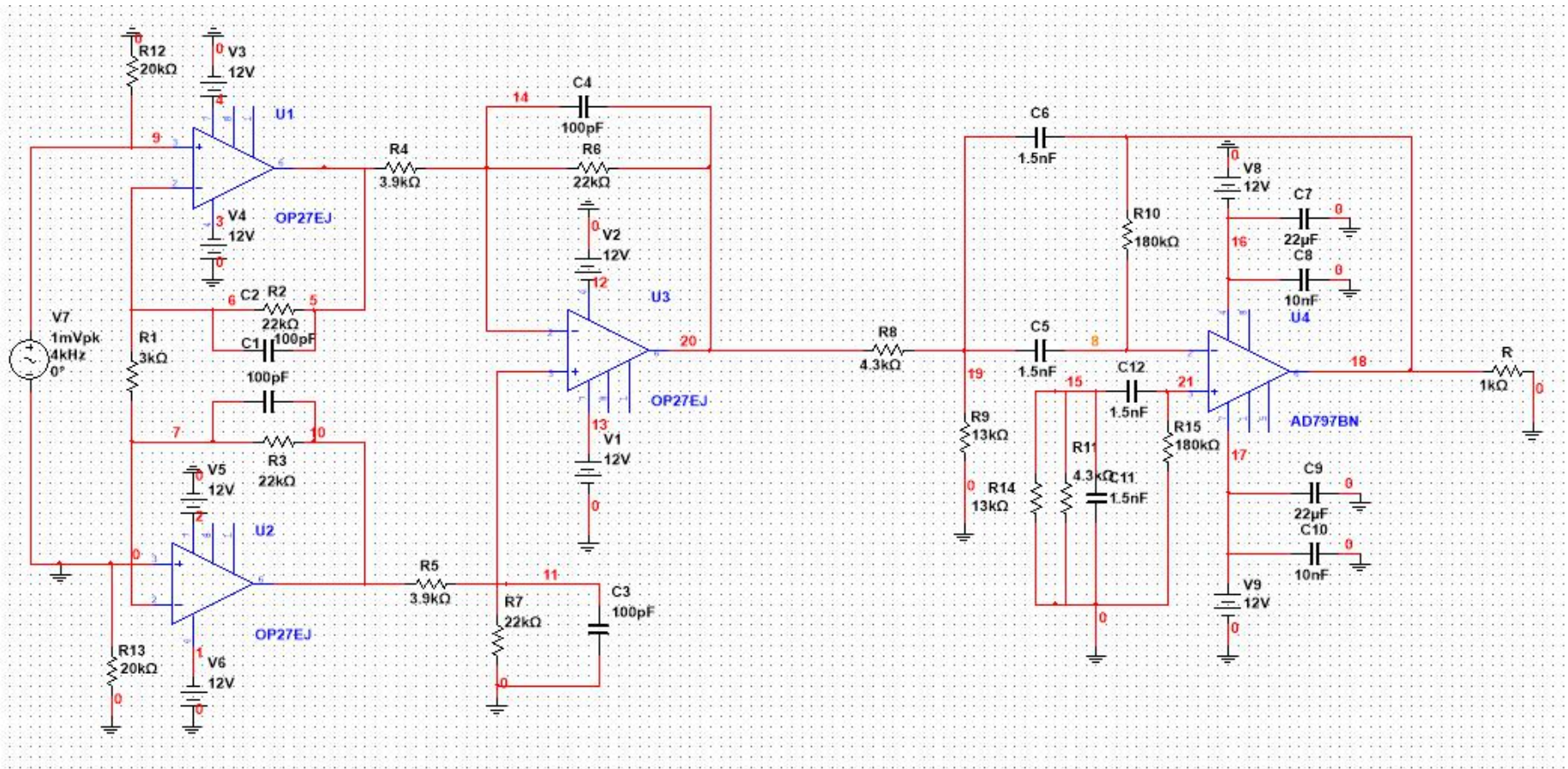





# Plan 2

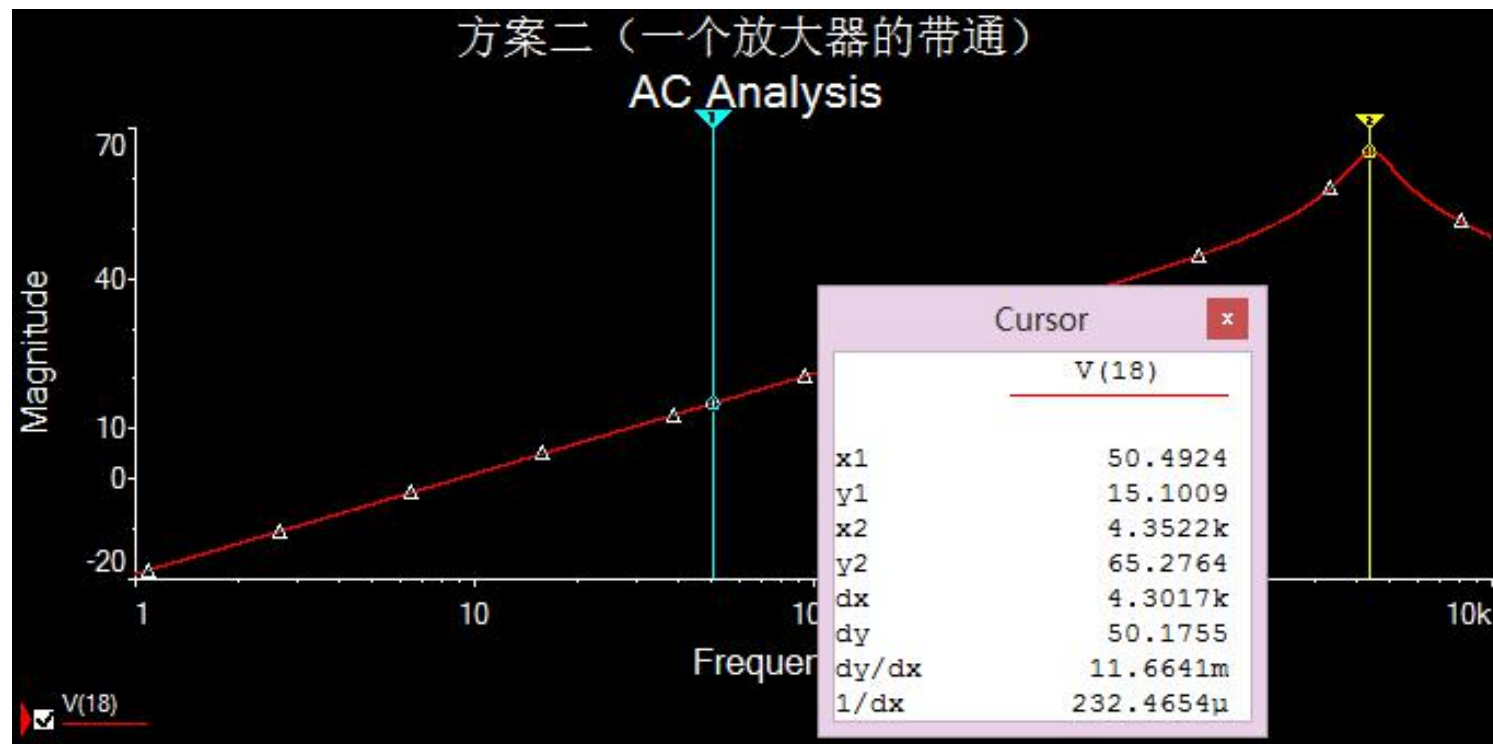


## OP27—Typical Performance Characteristics

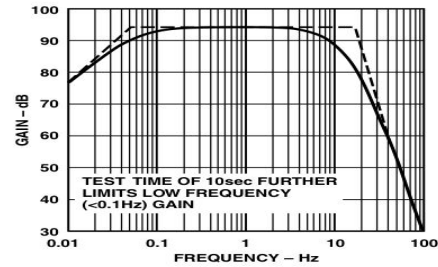


TPC 1. 0.1 Hz to 10 Hz<sub>p-p</sub> Noise Tester Frequency Response

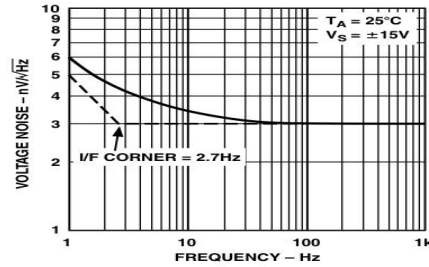


TPC 2. Voltage Noise Density vs. Frequency

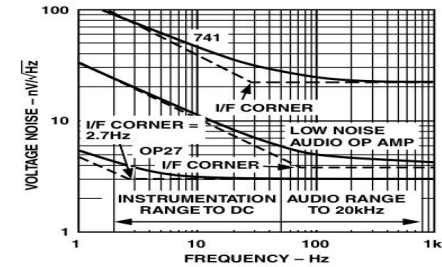


TPC 3. A Comparison of Op Amp Voltage Noise Spectra

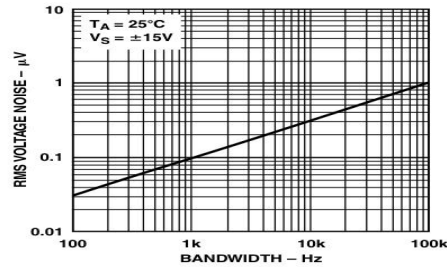


TPC 4. Input Wideband Voltage Noise vs. Bandwidth (0.1 Hz to Frequency Indicated)

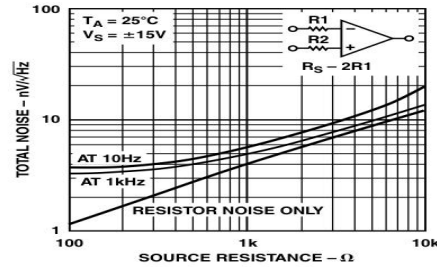


TPC 5. Total Noise vs. Sourced Resistance

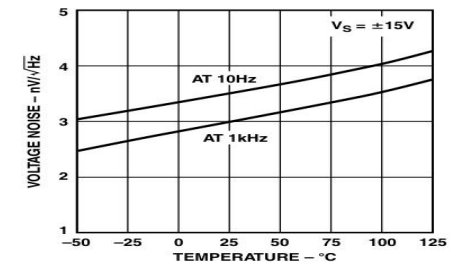


TPC 6. Voltage Noise Density vs. Temperature

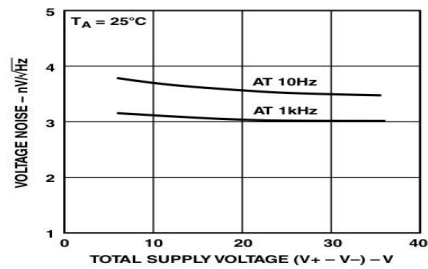

TPC 7. Voltage Noise Density vs. Supply Voltage

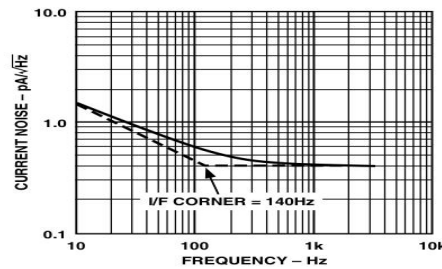

TPC 8. Current Noise Density vs. Frequency

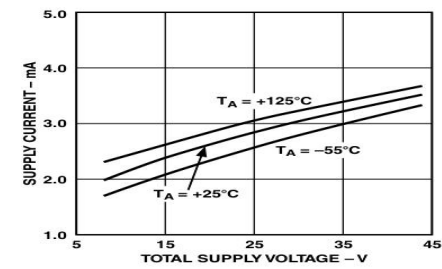

TPC 9. Supply Current vs. Supply Voltage



# Noise analysis plan 1

$$R_{eq}=1.468k\Omega$$

$$BW=1kHz$$

$$BW_n=1.57kHz$$

$$e_{nf} = 1.2 \times \sqrt{\ln(1.57kHz/0.1Hz)} nV = 3.7nV$$

$$e_{nBB} = e_{nBB} \times \sqrt{BW_n} = 3 \times \sqrt{1570} = 118.8nV$$

$$e_{n-v} = \sqrt{e_{nf}^2 + e_{nBB}^2} = 118.9nV$$

$$e_{n-i} = R_{eq} \times e_{nBB} \times \sqrt{BW_n} = 17.5nV$$

$$e_{n-R} = \sqrt{4KT R_{eq} BW_n} = 0.195\mu V$$

$$e_{n-RTL} = \sqrt{e_{n-v}^2 + e_{n-i}^2 + e_{n-R}^2} = 0.230\mu V$$

## 仪表放大器噪声

由于仪表放大器主要用于放大微小精密信号，因此，有必要了解所有相关噪声源的效应。  
仪表放大器模型如下面图1所示。

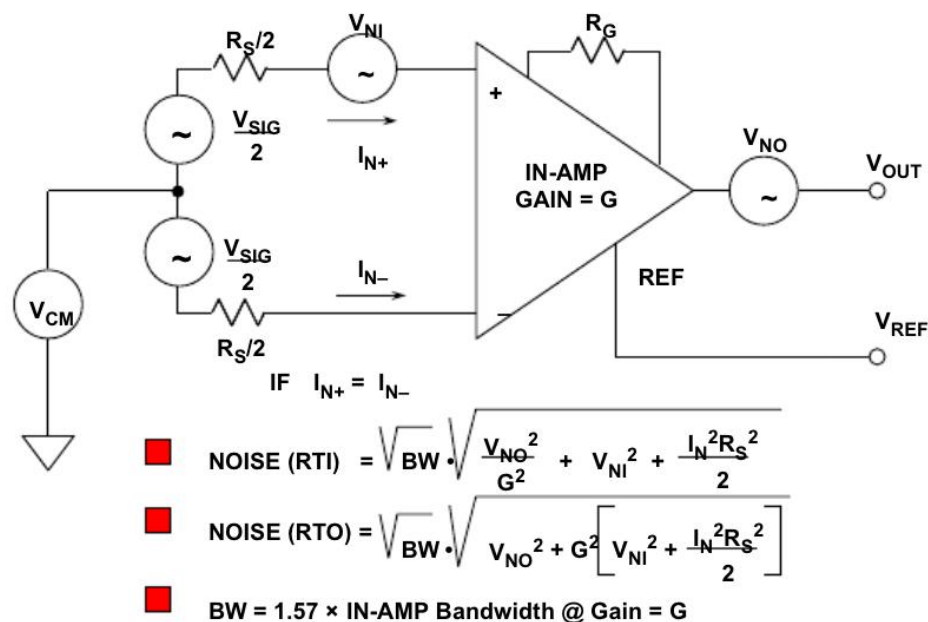


图1：仪表放大器噪声模型

# Noise analysis plan 2


$$RTI1 = \sqrt{BW_n} \times \sqrt{\frac{V_n^2}{G^2} + V_n^2 + \frac{I_n^2 R^2}{2}} = 914.39 \text{ nV}$$

$$(BW = 5 \text{ kHz } BW_n = 6.1 \text{ kHz})$$


$$RTI2 = 0.308 \text{ uV} / 11 = 28 \text{ nV}$$

$$RTI = 0.915 \text{ uV}$$



# PCB of Plan 1

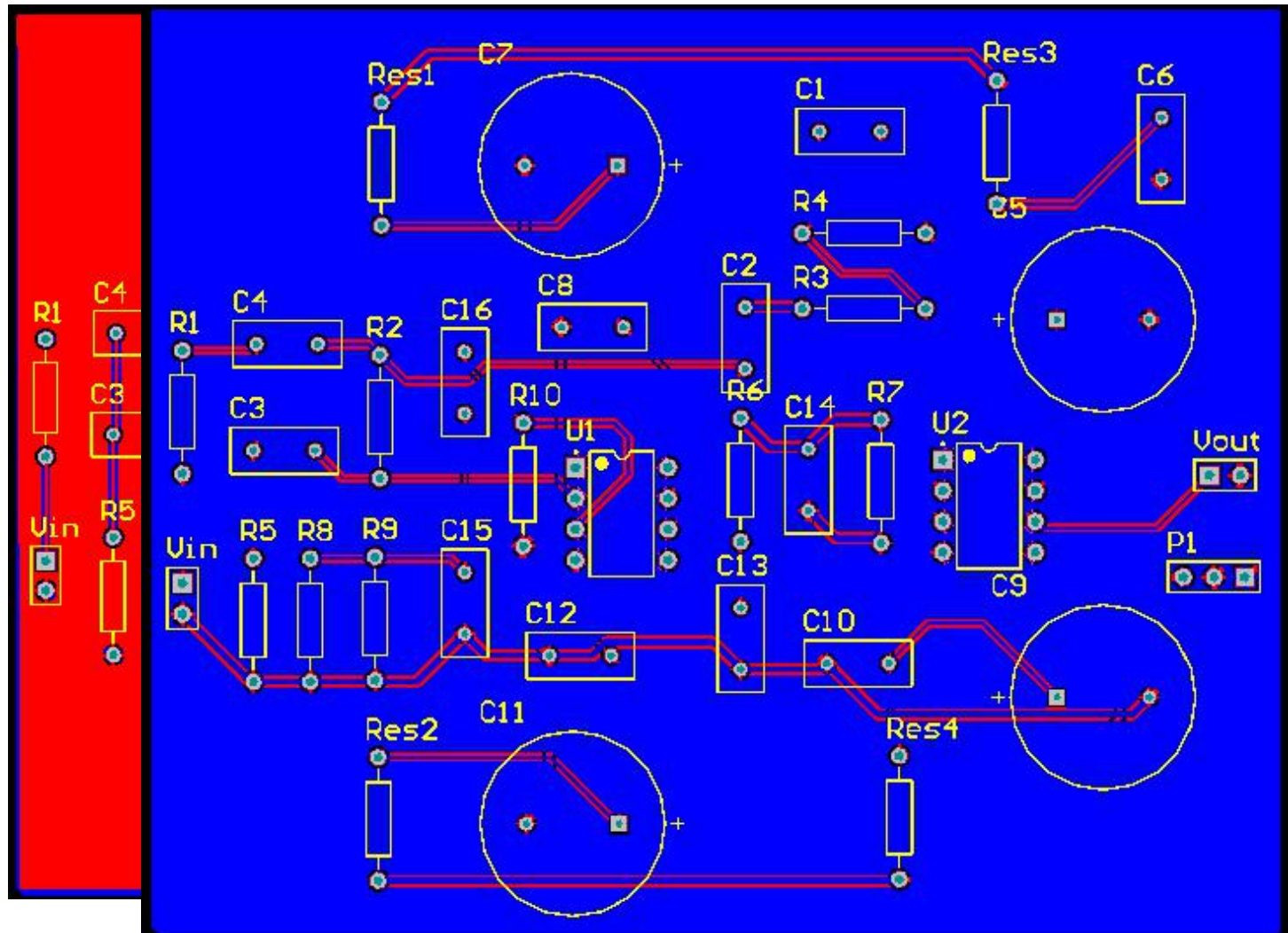

# PCB of Plan 2

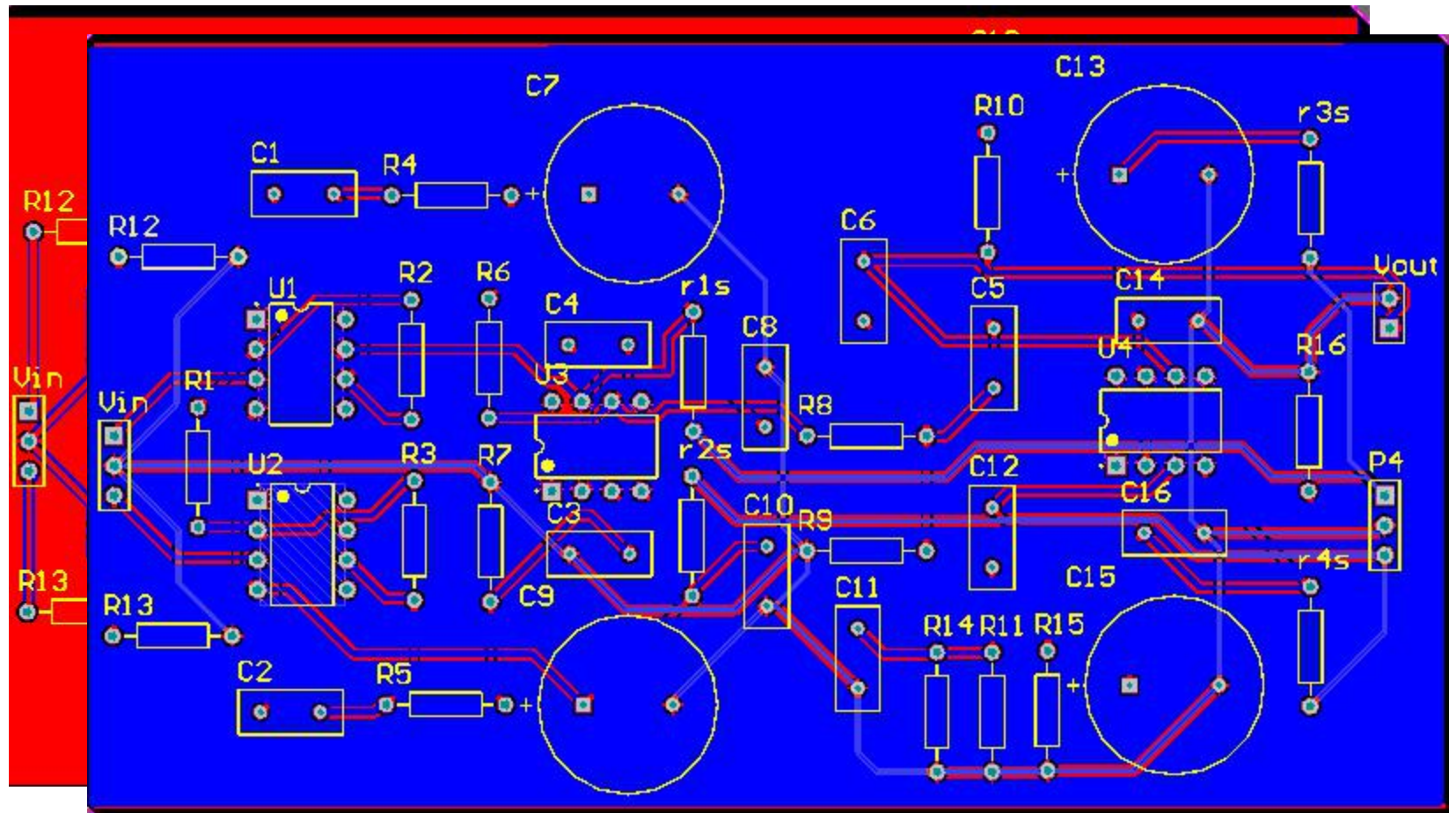


# Process

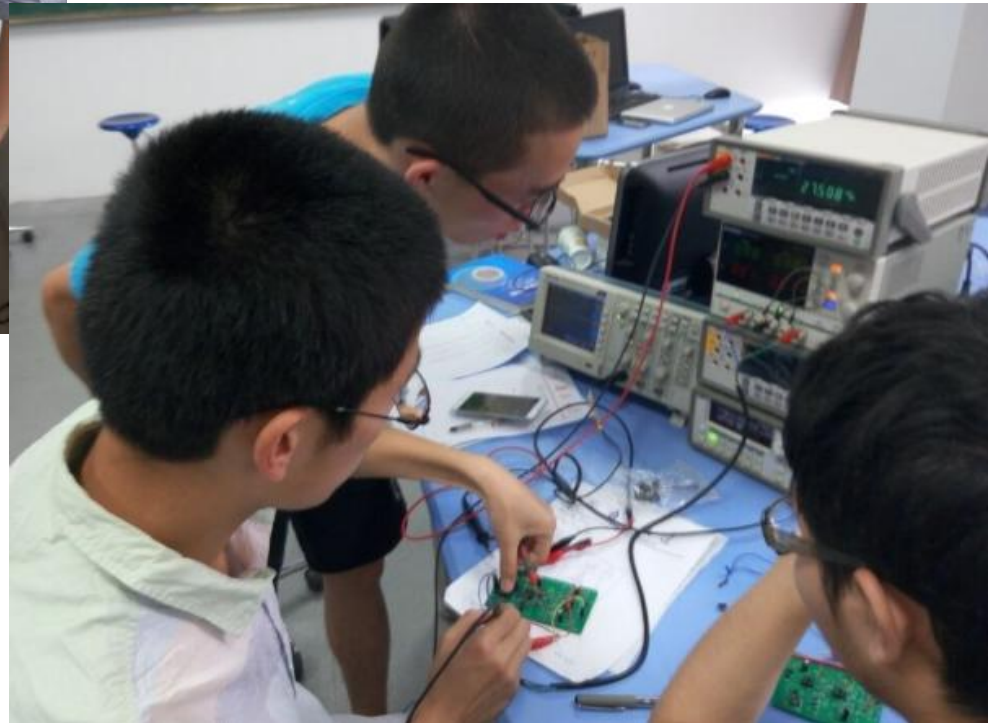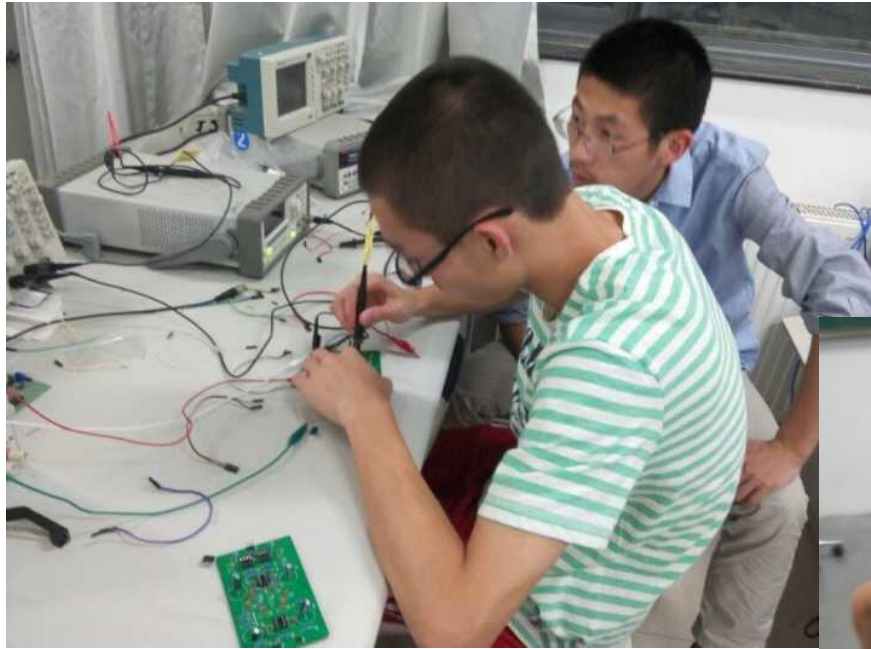




# Analysis of plan 1

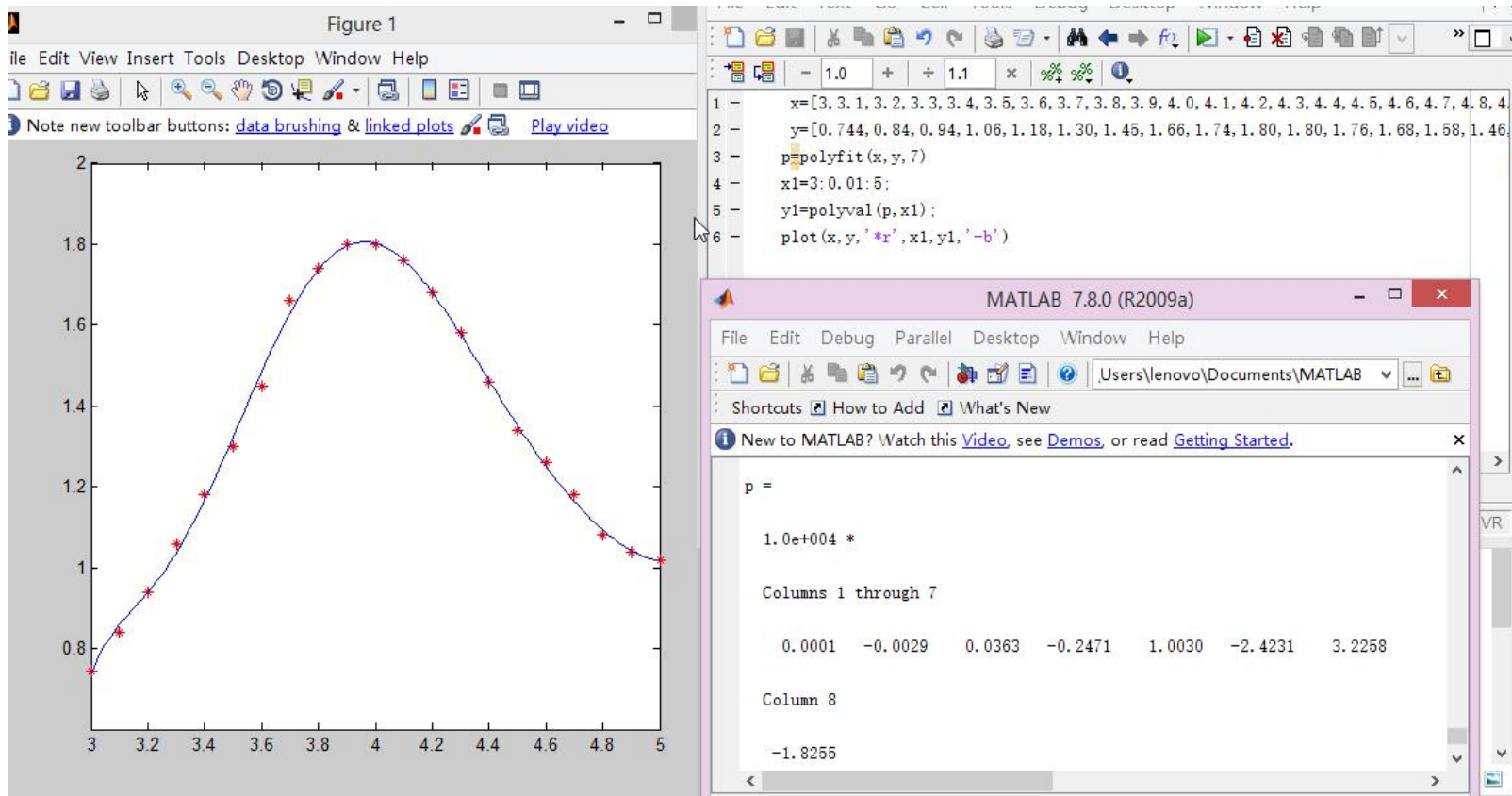

# Analysis of plan 2

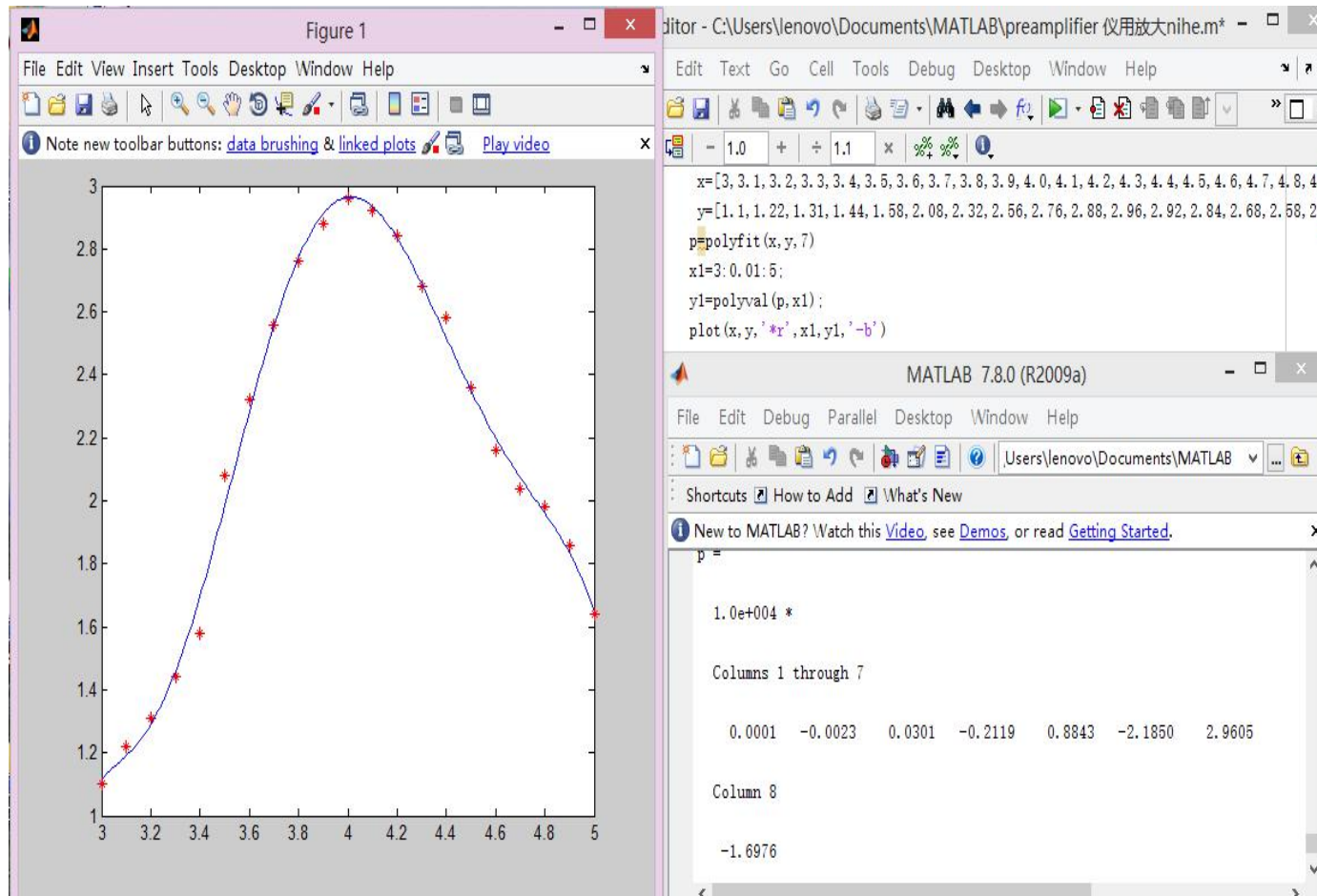

# Analysis

Plan 1	$f_0=4.0\text{kHz}$	(3.4kHz-4.6kHz)
	$A=1670$	
	$V_{\text{i-noise}}=62.6\mu\text{v}$	
plan2	$f_0=4.0\text{kHz}$	(3.5kHz-4.7kHz)
	$A=2040$	
	$V_{\text{i-noise}}=7.68\mu\text{v}$	

Thank you